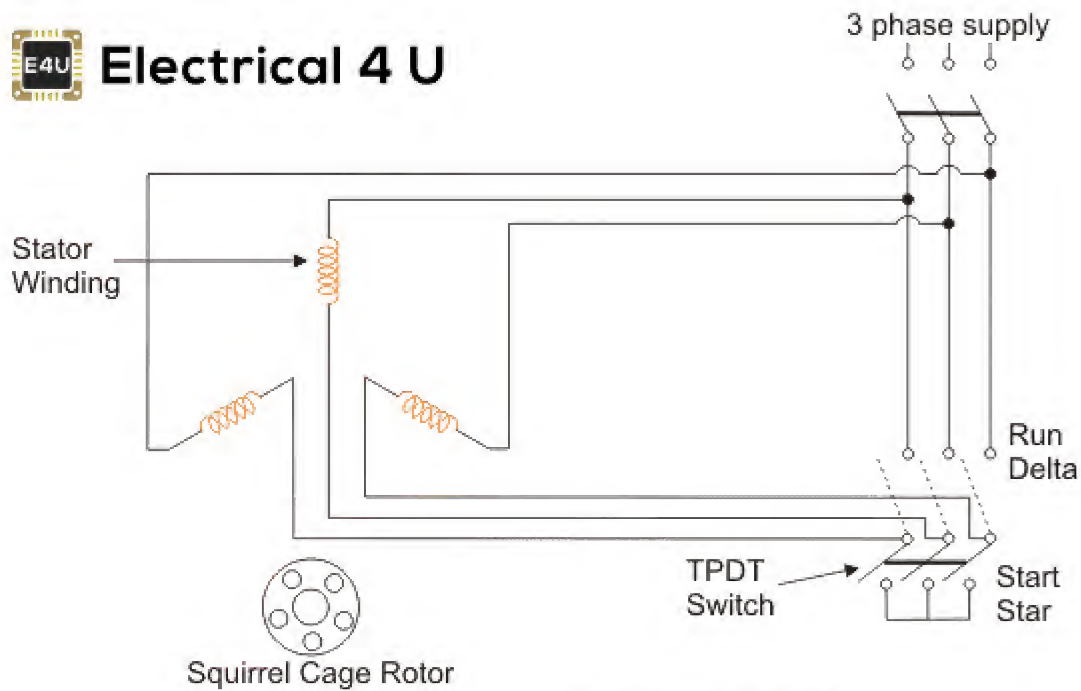




Electrical 4 U



Open-circuit Faults





(a). Single-phase open-circuit

(a). Two-phase open-circuit



(a). Three-phase open-circuit

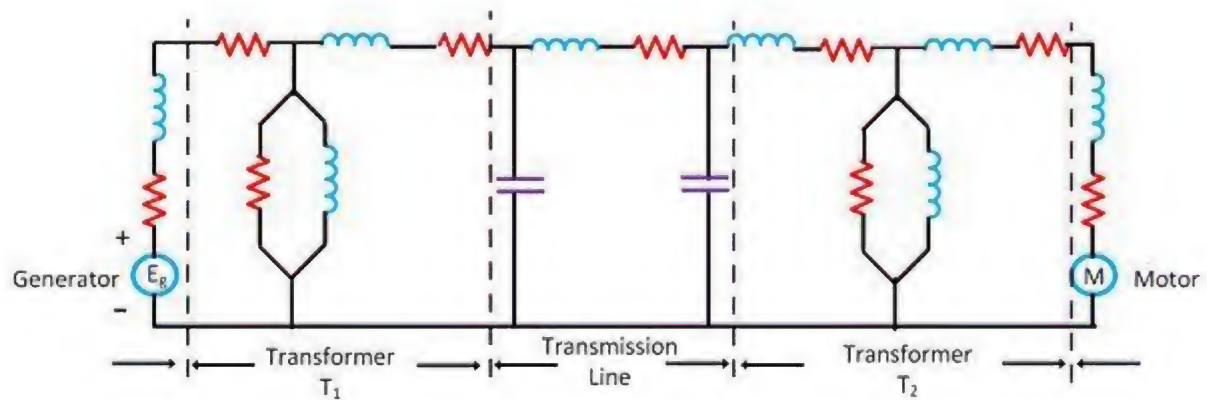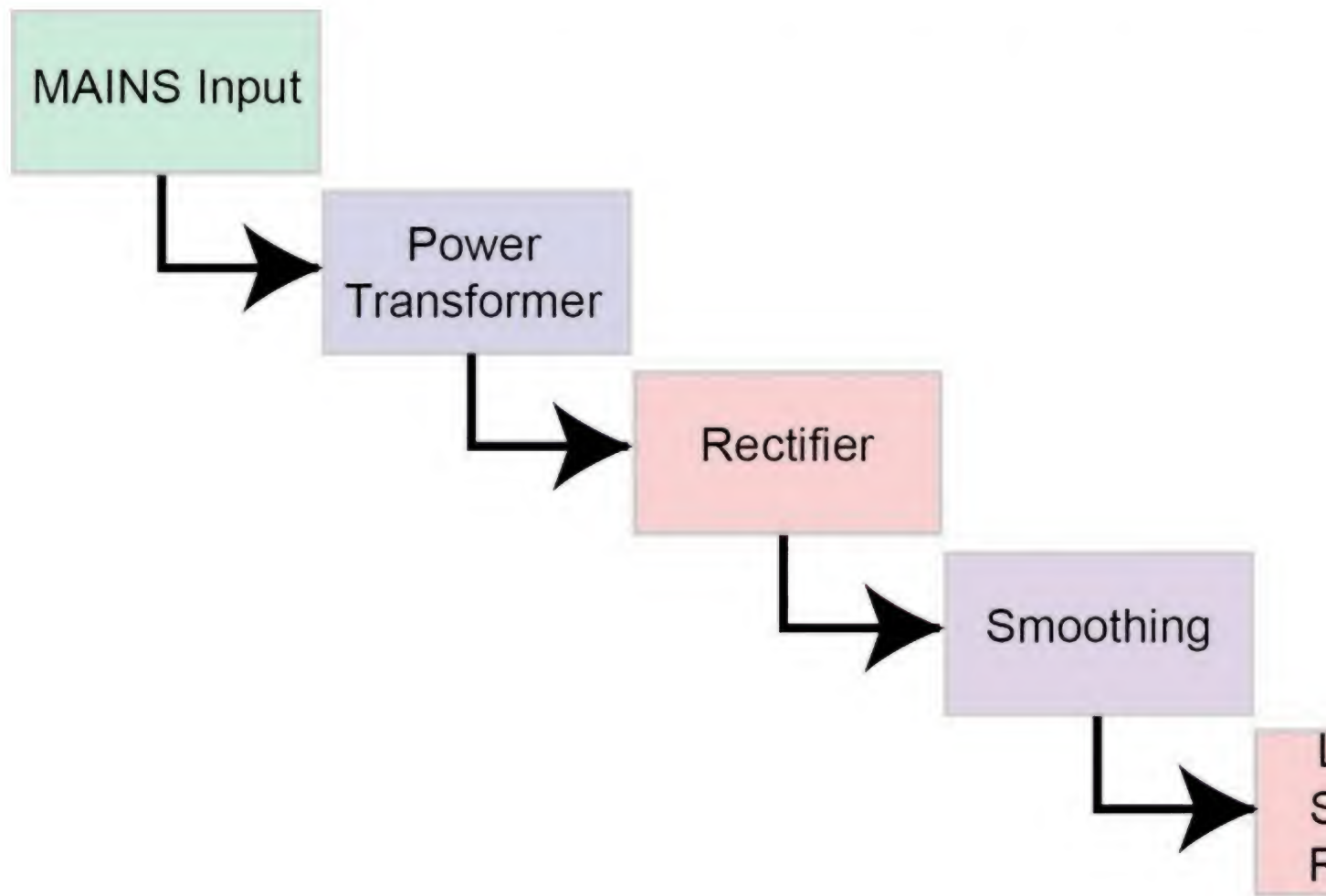

Impedance Diagram For The Power System

Circuit Globe

